

Digital System Design Assignment

A.H.T.M.Weerakoon
230689A

July 19, 2026

Contents

1	Exercise 1 : Sequence Detector (0110)	2
1.1	Objective	2
1.2	Verilog Code	2
1.3	Simulation Result	7
1.4	Maximum Supported Bit Rate	7
2	Exercise 2 : 32-bit Ripple Adder Using Four 8-bit Adders	8
2.1	Objective	8
2.2	Verilog Code	8
2.3	Simulation Result	16
2.4	Time Required for Four Additions	17
2.5	Pipelined 32-bit Adder	17
2.6	Advantages of Pipelining	17
3	Exercise 3 : 32-bit Carry Lookahead Adder	18
3.1	Objective	18
3.2	Verilog Code	18
3.3	Simulation Result	23
3.4	Performance Comparison	23
3.5	Comparison Table	23
4	Discussion	23
5	Conclusion	24

1 Exercise 1 : Sequence Detector (0110)

1.1 Objective

Design a sequence detector that detects the binary sequence **0110** for

- Overlapping detection
- Non-overlapping detection

1.2 Verilog Code

```
1
2 module seq_detector_overlap(
3     input logic clk,
4     input logic rst,
5     input logic x,
6     output logic y
7 );
8
9 typedef enum logic [2:0] {
10     S0, S1, S2, S3, S4
11 } state_t;
12
13 state_t state, next_state;
14
15 // State register
16 always_ff @(posedge clk or posedge rst) begin
17     if (rst)
18         state <= S0;
19     else
20         state <= next_state;
21 end
22
23 // Next-state logic
24 always_comb begin
25     case (state)
26
27         S0: begin
28             if (x)
29                 next_state = S0;
30             else
31                 next_state = S1;
32         end
33
34         S1: begin
35             if (x)
36                 next_state = S2;
37             else
38                 next_state = S1;
39         end

```

```

40
41     S2: begin
42         if (x)
43             next_state = S3;
44         else
45             next_state = S1;
46     end
47
48     S3: begin
49         if (x)
50             next_state = S0;
51         else
52             next_state = S4;
53     end
54
55     S4: begin
56         if (x)
57             next_state = S2;
58         else
59             next_state = S1;
60     end
61
62     default: next_state = S0;
63
64 endcase
65 end
66
67 // Output logic
68 assign y = (state == S4);
69
70 endmodule

```

Listing 1: Sequence Detector With Overlap

```

1
2 `timescale 1ns/1ps
3
4 module testbench;
5
6 logic clk;
7 logic rst;
8 logic x;
9 logic y;
10
11 seq_detector_overlap uut (
12     .clk(clk),
13     .rst(rst),
14     .x(x),
15     .y(y)
16 );
17

```

```

18 // Clock generation
19 always #5 clk = ~clk;
20
21 initial begin
22     clk = 0;
23     rst = 1;
24     x = 0;
25
26     #10 rst = 0;
27
28     // Input sequence: 0 1 1 0 1 1 0
29     x = 0; #10;
30     x = 1; #10;
31     x = 1; #10;
32     x = 0; #10;
33     x = 1; #10;
34     x = 1; #10;
35     x = 0; #10;
36
37     #20;
38     $finish;
39 end
40
41 initial begin
42     $dumpfile("dump.vcd");
43     $dumpvars(0, testbench);
44 end
45
46 endmodule

```

Listing 2: Testbench

```

1
2 module seq_detector_non_overlap(
3     input logic clk,
4     input logic rst,
5     input logic x,
6     output logic y
7 );
8
9 typedef enum logic [2:0] {
10     S0, S1, S2, S3, S4
11 } state_t;
12
13 state_t state, next_state;
14
15 // State register
16 always_ff @(posedge clk or posedge rst) begin
17     if (rst)
18         state <= S0;
19     else
20         state <= next_state;

```

```

21 end
22
23 // Next-state logic
24 always_comb begin
25     case (state)
26
27         S0: begin
28             if (x)
29                 next_state = S0;
30             else
31                 next_state = S1;
32         end
33
34         S1: begin
35             if (x)
36                 next_state = S2;
37             else
38                 next_state = S1;
39         end
40
41         S2: begin
42             if (x)
43                 next_state = S3;
44             else
45                 next_state = S1;
46         end
47
48         S3: begin
49             if (x)
50                 next_state = S0;
51             else
52                 next_state = S4;
53         end
54
55         S4: begin
56             if (x)
57                 next_state = S0;
58             else
59                 next_state = S1;
60         end
61
62         default: next_state = S0;
63
64     endcase
65 end
66
67 // Output logic
68 assign y = (state == S4);
69
70 endmodule

```

Listing 3: Sequence Detector Without Overlap

```

1
2 `timescale 1ns/1ps
3
4 module testbench;
5
6 logic clk;
7 logic rst;
8 logic x;
9 logic y;
10
11 seq_detector_non_overlap uut (
12     .clk(clk),
13     .rst(rst),
14     .x(x),
15     .y(y)
16 );
17
18 // Clock generation
19 always #5 clk = ~clk;
20
21 initial begin
22     clk = 0;
23     rst = 1;
24     x = 0;
25
26     #10 rst = 0;
27
28     // Input sequence: 0 1 1 0 1 0 1 1 0
29     x = 0; #10;
30     x = 1; #10;
31     x = 1; #10;
32     x = 0; #10;
33     x = 1; #10;
34     x = 0; #10;
35     x = 1; #10;
36     x = 1; #10;
37     x = 0; #10;
38
39     #20;
40     $finish;
41 end
42
43 initial begin
44     $dumpfile("dump.vcd");
45     $dumpvars(0, testbench);
46 end
47
48 endmodule

```

Listing 4: Testbench

1.3 Simulation Result

 


Figure 1: Simulation waveform for the overlapping sequence detector.

 


Figure 2: Simulation waveform for the non-overlapping sequence detector.

1.4 Maximum Supported Bit Rate

The maximum bit rate depends on the maximum operating clock frequency of the implemented design.

If

$$f_{max}$$

is the maximum clock frequency, then

$$\boxed{\text{Maximum Bit Rate} = f_{max} \text{ bits/s}}$$

because one input bit is processed during every clock cycle.

For example,

$$f_{max} = 100 \text{ MHz}$$

gives

$$\boxed{100 \text{ Mbit/s}}$$

The actual value depends on synthesis and FPGA timing analysis.

2 Exercise 2 : 32-bit Ripple Adder Using Four 8-bit Adders

2.1 Objective

Construct a 32-bit adder using four cascaded 8-bit ripple carry adders. Estimate the time required to add four pairs of 32-bit numbers. Then redesign the system using pipelining.

2.2 Verilog Code

```
1
2 `timescale 1ns/1ps
3
4 // 8-bit adder block
5 module adder8(
6     input  logic [7:0] A,
7     input  logic [7:0] B,
8     input  logic Cin,
9     output logic [7:0] Sum,
10    output logic Cout
11 );
12
13     assign {Cout, Sum} = A + B + Cin;
14
15 endmodule
16
17
18 // 32-bit adder using four cascaded 8-bit adders
19 module adder32_cascade(
20     input  logic [31:0] A,
21     input  logic [31:0] B,
22     output logic [31:0] Sum,
23     output logic Cout
24 );
25
26     logic c1, c2, c3;
27
28
29     adder8 add0(
30         .A(A[7:0]),
31         .B(B[7:0]),
32         .Cin(1'b0),
33         .Sum(Sum[7:0]),
34         .Cout(c1)
35     );
36
37
38     adder8 add1(
39         .A(A[15:8]),
40         .B(B[15:8]),
```



```

41         .Cin(c1),
42         .Sum(Sum[15:8]),
43         .Cout(c2)
44     );
45
46
47     adder8 add2(
48         .A(A[23:16]),
49         .B(B[23:16]),
50         .Cin(c2),
51         .Sum(Sum[23:16]),
52         .Cout(c3)
53     );
54
55
56     adder8 add3(
57         .A(A[31:24]),
58         .B(B[31:24]),
59         .Cin(c3),
60         .Sum(Sum[31:24]),
61         .Cout(Cout)
62     );
63
64 endmodule

```

Listing 5: 32-bit adder using four cascaded 8-bit adders

```

1
2 `timescale 1ns/1ps
3
4 module testbench;
5
6     logic [31:0] A;
7     logic [31:0] B;
8
9     logic [31:0] Sum;
10    logic Cout;
11
12
13    // Instantiate design
14    adder32_cascade DUT(
15        .A(A),
16        .B(B),
17        .Sum(Sum),
18        .Cout(Cout)
19    );
20
21
22    initial begin
23
24        $dumpfile("dump.vcd");

```

```

25     $dumpvars(0,testbench);
26
27
28     A = 32'd100;
29     B = 32'd50;
30
31     #10;
32
33     $display("A = %b",A);
34     $display("B = %b",B);
35     $display("SUM = %b",Sum);
36     $display("CARRY = %b",Cout);
37
38
39     A = 32'b1111111111111111111111111111110;
40     B = 32'b1000000000000000000000000000001;
41
42     #10;
43
44     $display("SUM = %b",Sum);
45     $display("CARRY = %b",Cout);
46
47
48     #10;
49     $finish;
50
51     end
52
53 endmodule

```

Listing 6: Testbench

```

1
2 `timescale 1ns/1ps
3
4
5 module adder8(
6     input  logic [7:0] A,
7     input  logic [7:0] B,
8     input  logic Cin,
9
10    output logic [7:0] Sum,
11    output logic Cout
12 );
13
14    assign {Cout,Sum} = A + B + Cin;
15
16 endmodule
17
18
19
20 module adder32_pipeline(

```

```

21
22     input logic clk,
23     input logic rst,
24
25     input logic [31:0] A,
26     input logic [31:0] B,
27
28     output logic [31:0] Sum,
29     output logic Cout
30 );
31
32
33 ///////////////////////////////////////////////////////////////////
34 // PIPELINE STAGE 1
35 // Add bits 7:0
36 ///////////////////////////////////////////////////////////////////
37
38 logic [7:0] s0;
39 logic c0;
40
41
42 adder8 add0(
43     .A(A[7:0]),
44     .B(B[7:0]),
45     .Cin(1'b0),
46     .Sum(s0),
47     .Cout(c0)
48 );
49
50
51 logic [7:0] sum0_reg;
52 logic carry0_reg;
53
54 logic [23:0] A1_reg;
55 logic [23:0] B1_reg;
56
57
58 always_ff @(posedge clk)
59 begin
60
61     sum0_reg    <= s0;
62     carry0_reg  <= c0;
63
64     A1_reg <= A[31:8];
65     B1_reg <= B[31:8];
66
67 end
68
69
70
71 ///////////////////////////////////////////////////////////////////

```

```

72 // PIPELINE STAGE 2
73 // Add bits 15:8
74 //////////////////////////////////////
75
76 logic [7:0] s1;
77 logic c1;
78
79
80 adder8 add1(
81     .A(A1_reg[7:0]),
82     .B(B1_reg[7:0]),
83     .Cin(carry0_reg),
84     .Sum(s1),
85     .Cout(c1)
86 );
87
88
89 logic [15:0] sum1_reg;
90
91 logic carry1_reg;
92
93 logic [15:0] A2_reg;
94 logic [15:0] B2_reg;
95
96
97 always_ff @(posedge clk)
98 begin
99
100     sum1_reg <= {s1,sum0_reg};
101
102     carry1_reg <= c1;
103
104     A2_reg <= A1_reg[23:8];
105     B2_reg <= B1_reg[23:8];
106
107 end
108
109
110
111 //////////////////////////////////////
112 // PIPELINE STAGE 3
113 // Add bits 23:16
114 //////////////////////////////////////
115
116 logic [7:0] s2;
117 logic c2;
118
119
120 adder8 add2(
121     .A(A2_reg[7:0]),
122     .B(B2_reg[7:0]),

```

```

123     .Cin(carry1_reg),
124     .Sum(s2),
125     .Cout(c2)
126 );
127
128
129 logic [23:0] sum2_reg;
130
131 logic carry2_reg;
132
133 logic [7:0] A3_reg;
134 logic [7:0] B3_reg;
135
136
137 always_ff @(posedge clk)
138 begin
139
140     sum2_reg <= {s2,sum1_reg};
141
142     carry2_reg <= c2;
143
144     A3_reg <= A2_reg[31:23];
145     B3_reg <= B2_reg[31:23];
146
147 end
148
149
150
151 ///////////////////////////////////////////////////
152 // PIPELINE STAGE 4
153 // Add bits 31:24
154 ///////////////////////////////////////////////////
155
156 logic [7:0] s3;
157 logic c3;
158
159
160 adder8 add3(
161     .A(A3_reg),
162     .B(B3_reg),
163     .Cin(carry2_reg),
164     .Sum(s3),
165     .Cout(c3)
166 );
167
168
169
170 ///////////////////////////////////////////////////
171 // OUTPUT REGISTER
172 ///////////////////////////////////////////////////
173

```

```

174 always_ff @(posedge clk)
175 begin
176
177     if(rst)
178     begin
179         Sum  <= 0;
180         Cout <= 0;
181     end
182
183     else
184     begin
185         Sum  <= {s3,sum2_reg};
186         Cout <= c3;
187     end
188
189 end
190
191
192 endmodule

```

Listing 7: 32-bit adder using pipeline

```

1
2 `timescale 1ns/1ps
3
4 module testbench;
5
6 logic clk;
7 logic rst;
8
9 logic [31:0] A;
10 logic [31:0] B;
11
12 logic [31:0] Sum;
13 logic Cout;
14
15
16 adder32_pipeline DUT(
17     .clk(clk),
18     .rst(rst),
19     .A(A),
20     .B(B),
21     .Sum(Sum),
22     .Cout(Cout)
23 );
24
25
26 always #5 clk = ~clk;
27
28
29 initial begin

```

```

30
31     $dumpfile("dump.vcd");
32     $dumpvars(0,testbench);
33
34
35     clk = 0;
36     rst = 1;
37
38     A = 0;
39     B = 0;
40
41
42     #12;
43     rst = 0;
44
45
46     // Apply input before clock edge
47
48     #3;
49     A = 100;
50     B = 50;
51
52
53     #10;
54     A = 200;
55     B = 300;
56
57
58     #10;
59     A = 1000;
60     B = 2000;
61
62
63     #10;
64     A = 4000;
65     B = 5000;
66
67
68     #10;
69     A = 0;
70     B = 0;
71
72
73     // Wait for pipeline output
74
75     repeat(6)
76     begin
77         @(posedge clk);
78
79         #1;
80

```

```

81     $display(
82         "Time=%0t   A=%d B=%d Sum=%d Carry=%b",
83         $time,A,B,Sum,Cout
84     );
85
86     end
87
88
89     $finish;
90
91 end
92
93
94 endmodule

```

Listing 8: Testbench

2.3 Simulation Result

 


Figure 3: Simulation waveform for the 32-bit adder using four cascaded 8-bit adders

 


Figure 4: Simulation waveform for the 32-bit adder using pipeline

2.4 Time Required for Four Additions

Assume

$$T_8$$

is the propagation delay of one 8-bit adder.
Since four 8-bit adders are cascaded,

$$T_{32} = 4T_8$$

For four independent additions,

$$T_{Total} = 4T_{32}$$

Therefore,

$$T_{Total} = 16T_8$$

2.5 Pipelined 32-bit Adder

The pipeline divides the 32-bit addition into four stages. Each stage performs one 8-bit addition.

After the pipeline is filled,

- One completed 32-bit addition is produced every clock cycle.
- Multiple input pairs are processed simultaneously.
- Throughput increases significantly.

For four independent additions,

$$T_{Total} = 4T_8 + 3T_8$$

Therefore,

$$T_{Total} = 7T_8$$

2.6 Advantages of Pipelining

- Higher throughput
- Better hardware utilization
- Reduced critical path
- Higher maximum clock frequency

3 Exercise 3 : 32-bit Carry Lookahead Adder

3.1 Objective

Build a 32-bit Carry Lookahead Adder using four 8-bit CLA blocks. Compare its performance with the cascaded ripple carry adder.

3.2 Verilog Code

```
1
2 //=====
3 // 8-bit Carry Lookahead Adder
4 //=====
5 module cla8 (
6     input  [7:0] A,
7     input  [7:0] B,
8     input      Cin,
9     output [7:0] Sum,
10    output      Cout,
11    output      P_block,
12    output      G_block
13 );
14
15 wire [7:0] P, G;
16 wire [8:0] C;
17
18 assign C[0] = Cin;
19
20 // Propagate and Generate
21 assign P = A ^ B;
22 assign G = A & B;
23
24 // Carry Lookahead Equations
25 assign C[1] = G[0] | (P[0] & C[0]);
26
27 assign C[2] = G[1]
28             | (P[1] & G[0])
29             | (P[1] & P[0] & C[0]);
30
31 assign C[3] = G[2]
32             | (P[2] & G[1])
33             | (P[2] & P[1] & G[0])
34             | (P[2] & P[1] & P[0] & C[0]);
35
36 assign C[4] = G[3]
37             | (P[3] & G[2])
38             | (P[3] & P[2] & G[1])
39             | (P[3] & P[2] & P[1] & G[0])
40             | (P[3] & P[2] & P[1] & P[0] & C[0]);
41
42 assign C[5] = G[4]
```

```

43         | (P[4] & G[3])
44         | (P[4] & P[3] & G[2])
45         | (P[4] & P[3] & P[2] & G[1])
46         | (P[4] & P[3] & P[2] & P[1] & G[0])
47         | (P[4] & P[3] & P[2] & P[1] & P[0] & C[0]);
48
49 assign C[6] = G[5]
50         | (P[5] & G[4])
51         | (P[5] & P[4] & G[3])
52         | (P[5] & P[4] & P[3] & G[2])
53         | (P[5] & P[4] & P[3] & P[2] & G[1])
54         | (P[5] & P[4] & P[3] & P[2] & P[1] & G[0])
55         | (P[5] & P[4] & P[3] & P[2] & P[1] & P[0] & C[0]);
56
57 assign C[7] = G[6]
58         | (P[6] & G[5])
59         | (P[6] & P[5] & G[4])
60         | (P[6] & P[5] & P[4] & G[3])
61         | (P[6] & P[5] & P[4] & P[3] & G[2])
62         | (P[6] & P[5] & P[4] & P[3] & P[2] & G[1])
63         | (P[6] & P[5] & P[4] & P[3] & P[2] & P[1] & G[0])
64         | (P[6] & P[5] & P[4] & P[3] & P[2] & P[1] & P[0] & C
[0]);
65
66 assign C[8] = G[7]
67         | (P[7] & G[6])
68         | (P[7] & P[6] & G[5])
69         | (P[7] & P[6] & P[5] & G[4])
70         | (P[7] & P[6] & P[5] & P[4] & G[3])
71         | (P[7] & P[6] & P[5] & P[4] & P[3] & G[2])
72         | (P[7] & P[6] & P[5] & P[4] & P[3] & P[2] & G[1])
73         | (P[7] & P[6] & P[5] & P[4] & P[3] & P[2] & P[1] & G
[0])
74         | (P[7] & P[6] & P[5] & P[4] & P[3] & P[2] & P[1] & P
[0] & C[0]);
75
76 assign Sum = P ^ C[7:0];
77 assign Cout = C[8];
78
79 // Block Propagate
80 assign P_block = &P;
81
82 // Block Generate
83 assign G_block =
84     G[7]
85     | (P[7]&G[6])
86     | (P[7]&P[6]&G[5])
87     | (P[7]&P[6]&P[5]&G[4])
88     | (P[7]&P[6]&P[5]&P[4]&G[3])
89     | (P[7]&P[6]&P[5]&P[4]&P[3]&G[2])
90     | (P[7]&P[6]&P[5]&P[4]&P[3]&P[2]&G[1])

```

```

91     | (P[7]&P[6]&P[5]&P[4]&P[3]&P[2]&P[1]&G[0]);
92
93 endmodule
94
95 //=====
96 // 32-bit Carry Lookahead Adder (4      8-bit CLA)
97 //=====
98 module cla32 (
99     input  [31:0] A,
100    input  [31:0] B,
101    input           Cin,
102    output [31:0] Sum,
103    output           Cout
104 );
105
106 wire [3:0] P, G;
107 wire [4:0] C;
108
109 assign C[0] = Cin;
110
111 // Lookahead carries between 8-bit blocks
112 assign C[1] = G[0] | (P[0] & C[0]);
113
114 assign C[2] = G[1]
115             | (P[1] & G[0])
116             | (P[1] & P[0] & C[0]);
117
118 assign C[3] = G[2]
119             | (P[2] & G[1])
120             | (P[2] & P[1] & G[0])
121             | (P[2] & P[1] & P[0] & C[0]);
122
123 assign C[4] = G[3]
124             | (P[3] & G[2])
125             | (P[3] & P[2] & G[1])
126             | (P[3] & P[2] & P[1] & G[0])
127             | (P[3] & P[2] & P[1] & P[0] & C[0]);
128
129 cla8 CLA0(
130     .A(A[7:0]),
131     .B(B[7:0]),
132     .Cin(C[0]),
133     .Sum(Sum[7:0]),
134     .Cout(),
135     .P_block(P[0]),
136     .G_block(G[0])
137 );
138
139 cla8 CLA1(
140     .A(A[15:8]),
141     .B(B[15:8]),

```

```

142     .Cin(C[1]),
143     .Sum(Sum[15:8]),
144     .Cout(),
145     .P_block(P[1]),
146     .G_block(G[1])
147 );
148
149 cla8 CLA2(
150     .A(A[23:16]),
151     .B(B[23:16]),
152     .Cin(C[2]),
153     .Sum(Sum[23:16]),
154     .Cout(),
155     .P_block(P[2]),
156     .G_block(G[2])
157 );
158
159 cla8 CLA3(
160     .A(A[31:24]),
161     .B(B[31:24]),
162     .Cin(C[3]),
163     .Sum(Sum[31:24]),
164     .Cout(),
165     .P_block(P[3]),
166     .G_block(G[3])
167 );
168
169 assign Cout = C[4];
170
171 endmodule

```

Listing 9: Carry Lookahead Adder

```

1
2 `timescale 1ns/1ps
3
4 module tb;
5
6 reg [31:0] A, B;
7 reg      Cin;
8
9 wire [31:0] Sum;
10 wire      Cout;
11
12 cla32 DUT (
13     .A(A),
14     .B(B),
15     .Cin(Cin),
16     .Sum(Sum),
17     .Cout(Cout)
18 );

```

```

19
20 initial begin
21     $dumpfile("dump.vcd");
22     $dumpvars(0,tb);
23
24     $display("
-----
");
25     $display("Time\tA\tB\tCin\tSum\tCout");
26     $display("
-----
");

27
28     A = 32'h00000000;
29     B = 32'h00000000;
30     Cin = 0;
31     #10;
32     $display("%0t\t%h\t%h\t%b\t%h\t%b", $time, A, B, Cin, Sum, Cout);
33
34     A = 32'h0000000F;
35     B = 32'h00000001;
36     Cin = 0;
37     #10;
38     $display("%0t\t%h\t%h\t%b\t%h\t%b", $time, A, B, Cin, Sum, Cout);
39
40     A = 32'h12345678;
41     B = 32'h87654321;
42     Cin = 0;
43     #10;
44     $display("%0t\t%h\t%h\t%b\t%h\t%b", $time, A, B, Cin, Sum, Cout);
45
46     A = 32'hFFFFFFFF;
47     B = 32'h00000001;
48     Cin = 0;
49     #10;
50     $display("%0t\t%h\t%h\t%b\t%h\t%b", $time, A, B, Cin, Sum, Cout);
51
52     A = 32'hAAAAAAAA;
53     B = 32'h55555555;
54     Cin = 1;
55     #10;
56     $display("%0t\t%h\t%h\t%b\t%h\t%b", $time, A, B, Cin, Sum, Cout);
57
58     #10;
59     $finish;
60 end
61
62 endmodule

```

Listing 10: Testbench

3.3 Simulation Result

 


Figure 5: Simulation waveform for Carry Lookahead Adder

3.4 Performance Comparison

Ripple Carry Adders propagate carries through every stage.

Therefore,

$$Delay \propto n$$

where n is the number of bits.

Carry Lookahead Adders compute carries in parallel using generate and propagate signals.

Hence,

$$Delay \ll n$$

resulting in significantly faster operation.

3.5 Comparison Table

Feature	Ripple Carry Adder	Carry Lookahead Adder
Carry Generation	Sequential	Parallel
Speed	Lower	Higher
Propagation Delay	High	Low
Hardware Complexity	Simple	Higher
Area	Smaller	Larger
Maximum Clock Frequency	Lower	Higher

Table 1: Comparison of Ripple Carry and Carry Lookahead Adders

4 Discussion

The sequence detector successfully identifies the required pattern for both overlapping and non-overlapping cases.

The cascaded ripple carry adder is simple to design but has a relatively large propagation delay because each carry must propagate through every 8-bit block.

Introducing pipelining increases throughput by allowing different input pairs to be processed simultaneously.

The Carry Lookahead Adder further improves performance by computing carry signals in parallel, reducing the critical path delay and increasing the maximum operating frequency.

5 Conclusion

In this assignment, three digital designs were implemented using Verilog.

The sequence detector demonstrated finite state machine implementation for overlapping and non-overlapping sequence detection.

The cascaded 32-bit ripple carry adder illustrated hierarchical design, while pipelining improved throughput significantly.

Finally, the Carry Lookahead Adder achieved superior performance by reducing carry propagation delay, making it more suitable for high-speed arithmetic applications.